



Q1

1. Pushing it to the Limit! [15 pts]

Prove that the short-circuit unity current gain (ω_T) of an NMOS transistor is $\frac{g_m}{(C_{gs} + C_{gd})}$. Neglect all extrinsic capacitors. (Hint: You will need to make an approximation; assume that the sC_{gd} term is small compared to g_m .)

$$\frac{I_o}{I_i}$$

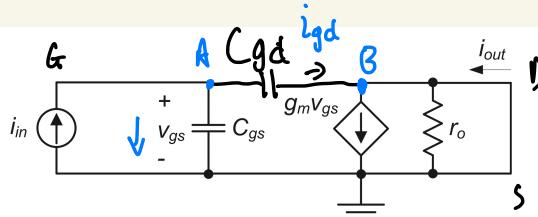


Figure 3-9: Small-signal circuit model for finding the MOSFET's transit frequency.


$$\frac{1}{j\omega C_s} = Z_C$$

$$\frac{1}{sC} = Z_C$$

C_{gd} is parallel with C_{gs}

$$C_{tot} = C_{gd} + C_{gs}$$

a) i_{out}

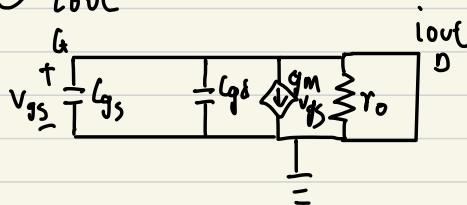

$$i_{out} = g_m V_{gs} = g_m i_{in} C_{tot}$$

$$= g_m i_{in} \frac{1}{s(C_{gd} + C_{gs})}$$

$$\left| \frac{i_{out}}{i_{in}} \right| = \frac{g_m}{s(C_{gd} + C_{gs})} = \frac{g_m}{j\omega(C_{gd} + C_{gs})} = 1$$


$$\omega_T = \frac{g_m}{C_{gs} + C_{gd}}$$

Q2

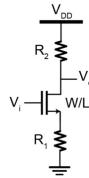2. Common-Source with Source Degeneration [25 pts]


Consider the circuit shown below.

- Draw the small-signal model of this circuit. Show that the small-signal dc-gain is $\frac{V_o}{V_i} = -\frac{g_m R_2}{1+g_m R_1}$ if the transistor is in saturation and the body is tied to the source.
- Redo part (a), but now tie the body to ground. (Note: The body is tied to the source for all other parts of this problem.)
- Calculate the maximum value of R_1 for each of the following bias currents: 50, 150, and 225 μ A. Use $R_1 = 8 \text{ k}\Omega$, $k_n = 125 \text{ }\mu\text{A/V}^2$, $W/L = 8$, and $V_{DD} = 5 \text{ V}$. Calculate the resulting small-signal gain for each current, assuming the transistor is in saturation.
- This circuit has a form of negative feedback. Show that the gain becomes independent of g_m under "strong feedback" where $g_m R_1 \gg 1$.
- Derive an expression for the circuit's output impedance (*i.e.*, the impedance seen looking into V_o). Take into account finite output impedance.



$$V_o = -g_m v_{gs} \cdot R_2$$

a)

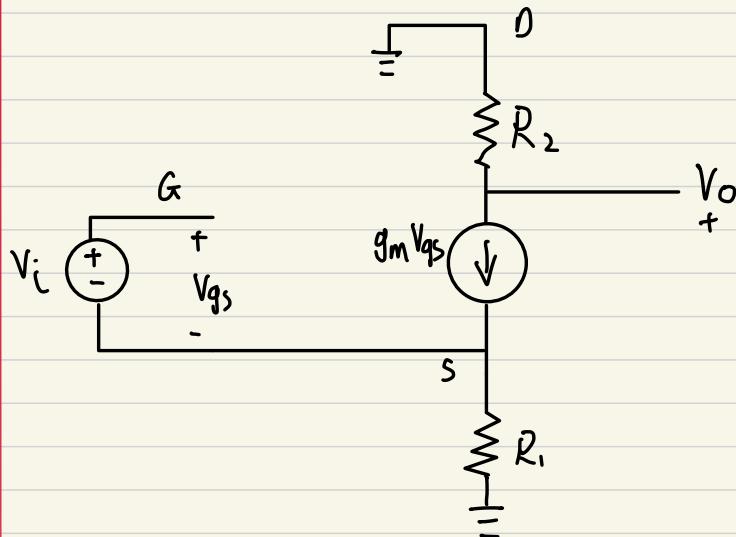

$$V_i = v_{gs} + g_m v_{gs} \cdot R_1$$

$$= v_{gs} (1 + g_m R_1)$$

$$\frac{V_o}{V_i} = \frac{-g_m v_{gs} R_2}{v_{gs} (1 + g_m R_1)} = \boxed{\frac{-g_m R_2}{1 + g_m R_1}}$$

$$V_o = -g_m v_{gs} \cdot R_2$$

b)


$$\frac{V_o}{R_2} = - (g_m V_{gs} + g_{mb} V_B)$$

$$\frac{V_S}{R_1} = (g_m V_{qs} + g_{mb} V_B) \quad \underline{\underline{=}}$$

$$V_{BS} = V_B - V_S$$

$$= -V_S$$

$$V_{qs} = V_i - V_S$$

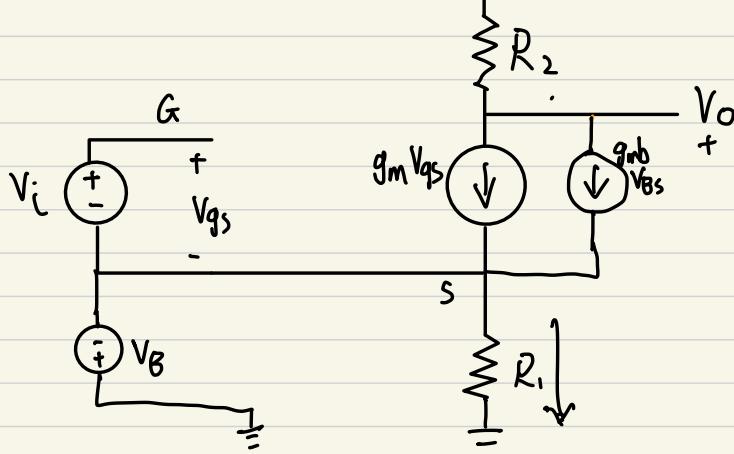

$$V_i = (g_m V_{qs} + g_{mb} (-V_S)) \cdot R_1 + V_{qs} \quad V_o = -(g_m V_{qs} + g_{mb} (-V_S)) \cdot R_2$$

$$V_S = V_i - V_{qs}$$

$$V_i = (g_m V_{qs} + g_{mb} (V_{qs} - V_i)) \cdot R_1 + V_{qs}$$

$$V_i = R_1 g_m V_{qs} + R_1 g_{mb} V_{qs} - R_1 g_{mb} V_i + V_{qs}$$

$$V_i (1 + R_1 g_{mb}) = V_{qs} (R_1 g_m + R_1 g_{mb} + 1)$$

$$V_i = \frac{V_{qs} (R_1 g_m + R_1 g_{mb} + 1)}{1 + R_1 g_{mb}}$$

$$V_o = - (g_m V_{qs} + g_{mb} (V_{qs} - V_i)) \cdot R_2$$

$$= -g_m V_{qs} \cdot R_2 - g_{mb} V_{qs} R_2 + g_{mb} V_i \cdot R_2$$

$$= -g_m V_{qs} \cdot R_2 - g_{mb} V_{qs} R_2 + g_{mb} (V_{qs} - \frac{R_1 V_o}{R_2}) \cdot R_2$$

$$V_o = -g_m V_{qs} \cdot R_2 - g_{mb} V_{qs} R_2 + g_{mb} V_{qs} R_2 - R_1 V_o \cdot g_{mb}$$

$$V_o(1 + R_1 g_{mb}) = V_{gs}(-g_m R_2 - g_{mb} R_2 + g_{mb} R_2)$$

$$V_o = \frac{V_{gs}(-g_m R_2)}{1 + R_1 g_{mb}}$$

$$\frac{V_o}{V_i} = \frac{V_{gs}(-g_m R_2)}{1 + R_1 g_{mb}} \cdot \frac{1 + R_1 g_{mb}}{V_{gs}(R_1 g_m + R_1 g_{mb} + 1)}$$

$$= \boxed{\frac{-g_m R_2}{g_m R_1 + g_{mb} R_1 + 1}}$$

$$C) I_D = 50 \mu A \quad R_1 = 8 k\Omega$$

$$I_0 = \frac{1}{2} k_n' \cdot \frac{w}{l} \cdot V_{DS}^2$$

$$V_{DS} = V_{GS} - V_t$$

$$V_s = V_{R_1} = I_D \cdot R_1 = 0.4 V$$

$$50 \mu A = \frac{1}{2} \cdot 125 \mu A \cdot 8 \cdot V_{DS}^2$$

$$V_{DS} = \frac{\sqrt{10}}{10} V \approx 0.316 V$$

$$g_m = \frac{2 I_D}{V_{DS}}$$

$$= \frac{2 \cdot 50 \mu A}{\frac{\sqrt{10}}{10}} \approx 3.16 \cdot 10^{-4}$$

Since in saturation $V_{DS} = V_{DS}$

$$\begin{aligned} V_{DS} &= V_D - V_s \\ \frac{\sqrt{10}}{10} V &= V_D - 0.4 V \\ V_D &= \frac{4 + \sqrt{10}}{10} V \end{aligned}$$

$$R_2 = \frac{V_{DD} - V_D}{I_D} = \frac{5 - \frac{4 + \sqrt{10}}{10}}{50 \mu A}$$

$$\approx 85.68 k\Omega$$

$$|A_V| = \left| -\frac{g_m R_2}{1 + g_m R_1} \right| = \frac{3.16 \cdot 10^{-4} \cdot 85.68 k\Omega}{1 + 3.16 \cdot 10^{-4} \cdot 8 k\Omega} \approx 7.68$$

$$I_D = 150 \mu A \quad V_s = I_D \cdot R_1 = 1.2 V$$

$$150 \mu A = \frac{1}{2} \cdot 125 \mu A \cdot 8 \cdot V_{DS}^2$$

$$V_{DS} = \frac{\sqrt{30}}{10} V$$

$$\begin{aligned} V_{DS} &= V_D - V_s \\ \frac{\sqrt{30}}{10} V &= V_D - 1.2 V \end{aligned}$$

$$R_2 = \frac{5 - \frac{12 + \sqrt{30}}{10}}{150 \mu A} \approx 21.68 k\Omega$$

$$V_D = \frac{12 + \sqrt{30}}{10}$$

$$|A_V| = \left| \frac{g_m R_2}{1 + g_m R_1} \right|$$

$$g_m = \frac{2 \cdot 150 \mu A}{\frac{\sqrt{30}}{10}} = 5.477 \cdot 10^{-4}$$

$$= \frac{5.477 \cdot 10^{-4} \cdot 21.68 k\Omega}{1 + 5.477 \cdot 10^{-4} \cdot 8 k\Omega}$$

$$\approx 2.21$$

$$I_0 = 225 \text{ uA} \quad V_s = I_0 \cdot R_1 = 1.8 \text{ V}$$

$$225 \text{ u} = \frac{1}{2} \cdot 125 \text{ u} \cdot 8 \cdot V_{ov}^2$$
$$V_{ov} = \frac{3\sqrt{5}}{10} \text{ V}$$

$$V_{DS} = V_D - V_s$$
$$\frac{3\sqrt{5}}{10} = V_D - 1.8$$

$$R_2 = \frac{5 - \frac{18 + 3\sqrt{5}}{10}}{225 \text{ u}} \approx 11.24 \text{ k}\Omega$$

$$V_D = \frac{18 + 3\sqrt{5}}{10}$$

$$|A_v| = \frac{g_m R_2}{1 + g_m R_1}$$

$$g_m = \frac{2 \cdot 225 \cdot u}{3\sqrt{5}}$$

$$= \frac{6.71 \cdot 10^{-4} \cdot 11.24 \text{ k}}{1 + 6.71 \cdot 10^{-4} \cdot 8 \text{ k}}$$

$$\approx 6.71 \cdot 10^{-4}$$

$$\approx 1.18$$

d) Based on the gain from a

$$\frac{V_o}{V_i} = -\frac{g_m R_2}{1 + g_m R_1}$$

when $g_m R_1 \gg 1$

$$\frac{V_o}{V_i} = -\frac{g_m R_2}{g_m R_1} \Rightarrow g_m \text{ is canceled} = \frac{-R_2}{R_1}$$

The gain becomes independent of g_m

c)

Looking into V_O

V_i is grounded


$$V_{GS} = V_g - V_s$$

$$V_{GS} = -V_s$$

$$V_{GS}$$

$$V_s = g_m V_{GS} R_L$$
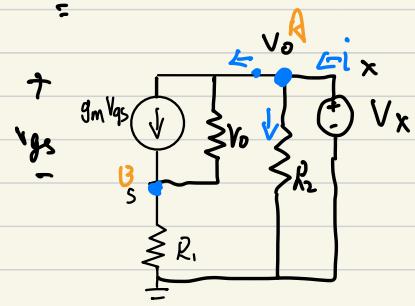
$$R_{eq} = \frac{V_x}{i_x} \quad i_x = -g_m V_{GS}$$



@ A

$$i_o = \frac{V_0}{R_2} + \frac{V_{GS}}{r_o} + g_m V_{GS}$$

$$@ B \quad g_m V_{GS} + \frac{V_{GS}}{r_o} = \frac{V_0 - V_{GS}}{R_2}$$

$$R_1 g_m V_{GS} + \frac{R_1 V_{GS}}{r_o} = V_0 - V_{GS}$$

$$V_{GS} \left(1 + R_1 g_m + \frac{R_1}{r_o} \right) = V_0$$

$$\begin{aligned} i_o &= \frac{V_0}{R_2} + \frac{V_0}{\left(1 + R_1 g_m + \frac{R_1}{r_o} \right) r_o} + g_m \frac{V_0}{\left(1 + R_1 g_m + \frac{R_1}{r_o} \right)} \\ &= V_0 \left(\frac{1}{R_2} + \frac{1}{\left(1 + R_1 g_m + \frac{R_1}{r_o} \right) r_o} + \frac{g_m}{\left(1 + R_1 g_m + \frac{R_1}{r_o} \right)} \right) \end{aligned}$$

$$i_o = V_0 \left(\frac{\left(1 + R_1 g_m + \frac{R_1}{r_o} \right) r_o + R_2 + R_2 r_o g_m}{R_2 \cdot \left(1 + R_1 g_m + \frac{R_1}{r_o} \right) r_o} \right)$$

$$\frac{V_0}{i_o} = \boxed{\frac{R_2 \cdot \left(1 + R_1 g_m + \frac{R_1}{r_o} \right) r_o}{\left(1 + R_1 g_m + \frac{R_1}{r_o} \right) r_o + R_2 + R_2 r_o g_m}}$$

Q3

a)

Assume M_2 also in saturation

M_3 : Will be in saturation

since $V_{DS} = V_{GS}$, then $V_{DS} > V_{GS} - V_t$

$$V_{GS} - V_t = 3.5 - V_o - V_t > 0$$

$$3.5 - V_t > V_o$$

$$V_o < 3.5 - V_t$$

$$M_2: V_{DS} = V_o - V_{o_2} \quad V_o + V_t < 3.5$$

$$V_{GS} = V_I - V_{o_2}$$

$$V_{DS} > V_{GS} - V_t \Rightarrow V_o - V_{o_2} > V_I - V_{o_2} - V_t$$

$$V_o + V_t > V_I$$

M_1 : will be in saturation as well, since $V_{DS} = V_{GS}$, then $V_{DS} > V_{GS} - V_t$, However $V_{GS} - V_t > 0$

$$V_{GS,1} = V_{o_2} = V_{DS,1} > V_t$$

$$\text{In } M_2 \quad V_{GS,2} - V_t > 0 = V_I - V_{o_2} - V_t > 0$$


$$= V_I - V_{DS,1} - V_t > 0$$

$$\text{so } V_I > V_{DS,1} + V_t > V_I + V_t$$


$$2V_t < V_o + V_t < V_I < V_o + V_t < 3.5$$

Based on the range of V_I above

$$V_t < V_o < 3.5 - V_t$$

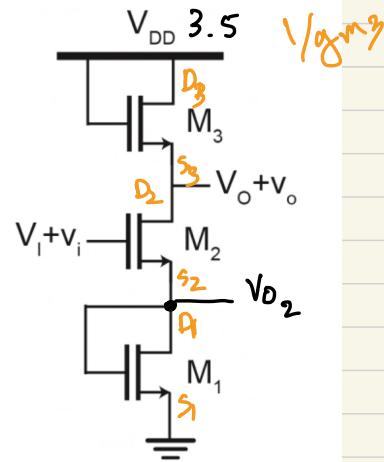

b)

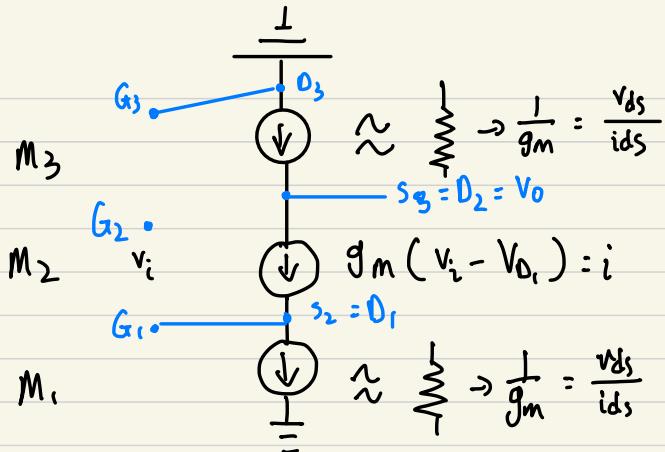

$$V_i = (V_i - V_{ds2}) + g_m (V_i - V_{ds2}) \cdot \frac{1}{g_m}$$

$$\left| \frac{V_0}{V_i} \right| = \left| \frac{- (V_i - V_{ds2})}{2 (V_i - V_{ds2})} \right| = 0.5$$

C)

$$V_{OV} = V_{GS} - V_t \Rightarrow V_{GS} = 450mV$$

$$\begin{aligned} M_3: I_{D_3} &= \underbrace{\frac{1}{2} \cdot k_n' \cdot \frac{W}{L}}_A \cdot (V_{GS} - V_t)^2 & V_{DS} > V_{OV} \\ &= A (V_{DD} - V_0 - V_t)^2 & V_{GS} = V_{DD} - V_0 \end{aligned}$$

$$M_2: I_{D_2} = A \cdot (V_I - V_{O_2} - V_t)^2 \quad V_{GS} = V_I - V_{O_2}$$

$$M_3: I_{D_1} = A \cdot (V_{O_2} - V_t)^2$$

$$I_{D_3} = I_{D_2} = I_{D_1}$$

$$V_{OD} - V_0 - V_t = V_I - V_{O_2} - V_t = V_{O_2} - V_t = 150mV$$

$$\begin{array}{ll} \textcircled{1} \quad V_{DD} - V_0 - 300mV = 150mV & \textcircled{2} \quad V_I - V_{O_2} = 450mV \\ V_{DD} - V_0 = 450mV & \textcircled{3} \quad V_{O_2} = 450mV \end{array}$$

$$\text{Use } \textcircled{3} \text{ solve } \textcircled{2} \rightarrow V_I = 900mV$$

$$V_{DS} \geq V_{OV}$$

$$V_0 - V_{O_2} = 150mV$$

$$V_0 = 600mV$$

Use $\textcircled{1}$


$$V_{DD} - V_0 = 450mV \Rightarrow V_{DD} = 1.05V$$

Check:

$$\checkmark M_3 \quad V_{DS} = 1.05 - 0.6 = 450mV \geq 150mV$$

$$\checkmark M_2 \quad V_{DS} = 600mV - 450mV \geq 150mV$$
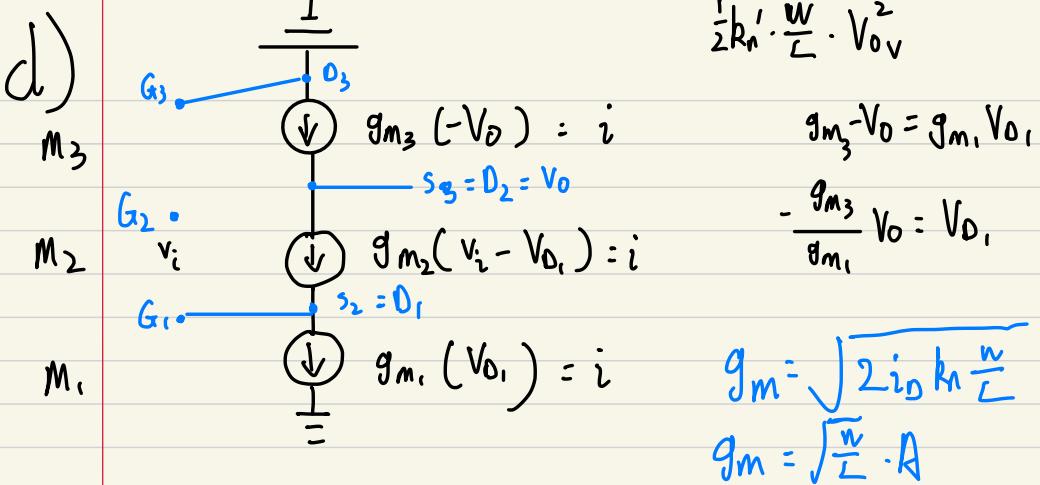
$$\checkmark M_1 \quad V_{DS} = 450mV \geq 450mV - 300mV$$



$$V_{D1} = \left(\frac{g_{m_2}}{g_{m_1} + g_{m_2}} \right) V_i$$

$$-g_{m_3} V_o = g_{m_2} \left(V_i - V_i \frac{g_{m_2}}{g_{m_1} + g_{m_2}} \right)$$

$$-g_{m_3} V_o = V_i \left(g_{m_2} - \frac{g_{m_2}^2}{g_{m_1} + g_{m_2}} \right)$$

$$\left| \frac{V_o}{V_i} \right| = \left| \frac{-1}{g_{m_3}} \left(g_{m_2} - \frac{g_{m_2}^2}{g_{m_1} + g_{m_2}} \right) \right| = 5$$

$$g_{m_2} - \frac{g_{m_2}^2}{g_{m_1} + g_{m_2}} = 5g_{m_3}$$

$$\frac{g_{m_2}(g_{m_1} + g_{m_2}) - g_{m_2}^2}{g_{m_1} + g_{m_2}} = 5g_{m_3}$$

$$\frac{g_{m_1} g_{m_2}}{g_{m_1} + g_{m_2}} = 5g_{m_3}$$

$$\frac{\sqrt{10} g_{m_1}}{\sqrt{10} + g_{m_1}} = 5g_{m_3}$$

$$\frac{\sqrt{10} g_{m_1}}{\sqrt{10} + g_{m_1}} = 5g_{m_3}$$

$$\text{Let's assume } g_{m_1} = \sqrt{35} \cdot A \Rightarrow \left(\frac{w}{l}\right)_1 = 35$$

then solving above equation, we get

$$g_{m_3} = \frac{-2\sqrt{35} + 7\sqrt{10}}{2.5} \cdot A$$

$$\left(\frac{w}{l}\right)_3 \approx 0.17$$


This wouldn't change the requirement in part c), since we only change the $\left(\frac{w}{l}\right)$ ratio to maintain same current across each transistor

Q4

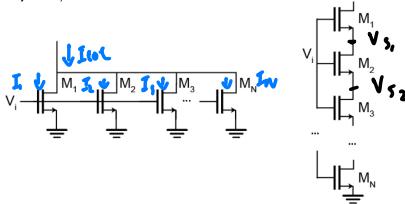4. Parallel/Series Transistors [20 pts]

Consider the circuits shown below. Each transistor has the same W/L .

- Derive an expression for W and L for a single transistor that replaces, and is equivalent to, the multiple transistors. (Note: Neglect the body effect.)
- For the parallel transistors, re-derive (a) without requiring all the transistors to have the same W .
- For the series transistors, re-derive (a) without requiring all the transistors to have the same L . (Note: Neglect the body effect.)



a)

Parallel:

For M_1 to M_N

$$I_D = \frac{1}{2} k_n' \cdot \frac{W}{L} (V_i - V_t)^2 = \underbrace{\sum_{i=1}^N k_n' (V_i - V_t)^2}_{A} \cdot \frac{W}{L}$$

A is the same for all transistors

$$\begin{aligned} I_{\text{tot}} &= I_1 + I_2 + I_3 + \dots + I_N \\ &= A \cdot \frac{W_1}{L_1} + A \cdot \frac{W_2}{L_2} + A \cdot \frac{W_3}{L_3} + \dots + A \cdot \frac{W_N}{L_N} \end{aligned}$$

$$\text{Since } \frac{W_1}{L_1} = \frac{W_2}{L_2} = \dots = \frac{W_N}{L_N}$$

$$I_{\text{tot}} = A \frac{W}{L} \cdot N$$

Replace all transistors with single one

$$I_{\text{tot}} = A \cdot \left(\frac{W}{L}\right)_{\text{eq}} = A \cdot \frac{W}{L} \cdot N$$

$$\text{So } \left(\frac{W}{L}\right)_{\text{eq}} = N \cdot \frac{W}{L}$$

Series

$$M_1: I_D = \frac{1}{2} k_n' \frac{w}{l} (V_{GS} - V_t)^2$$

$$= \frac{1}{2} k_n' \frac{w}{l} (V_i - V_{S1} - V_t)^2$$

$$M_2: k_n \frac{w}{l} ((V_i - V_t) \cdot V_{S1} - \frac{1}{2} V_{S1}^2)$$

$$V_i - V_{S1} - V_t > 0$$

$$V_i - V_t > V_{S1}$$

$$V_{S2} = V_{DS2}$$

$$V_{GS} - V_t = V_{DS}$$

$$V_i - V_t = V_{DS}$$

If M_2 in Sat, then M_1 is in cutoff

If M_1 in Sat, then M_2 : $V_{DS2} = V_{S1}$ in Triode Region

$$\begin{aligned} &\Downarrow \\ V_i - V_{S1} - V_t &> 0 \\ V_i - V_t &> V_{S1} \end{aligned}$$

$$\begin{aligned} &\Downarrow \\ V_{DS2} &< (V_{GS2} = V_i - V_t) \\ V_{S1} &< V_i - V_t \end{aligned}$$

$$\begin{aligned} I_D &= \frac{1}{2} k_n' \frac{w}{l} (V_i - V_{S1} - V_t)^2 = k_n \frac{w}{l} ((V_i - V_t) \cdot V_{S1} - \frac{1}{2} V_{S1}^2) \\ &= \frac{1}{2} \frac{w}{l} (V_i^2 - 2V_i V_{S1} - 2V_i V_t + V_{S1}^2 + 2V_{S1} V_t + V_t^2) \\ &= \frac{w}{l} (V_i V_{S1} - V_t V_{S1} - \frac{1}{2} V_{S1}^2) \quad \text{brace} \\ &= \frac{1}{2} V_i^2 - V_i V_{S1} - V_i V_t + \frac{1}{2} V_{S1}^2 + V_{S1} V_t + \frac{1}{2} V_t^2 \quad \text{brace} \\ &= V_i V_{S1} - V_t V_{S1} - \frac{1}{2} V_{S1}^2 \quad \text{brace} \\ &= \frac{1}{2} V_i^2 - 2V_i V_{S1} - V_i V_t + V_{S1}^2 + 2V_t V_{S1} + \frac{1}{2} V_t^2 \\ &= \frac{1}{2} (V_i - V_t)^2 - 2V_i V_{S1} + V_{S1}^2 + 2V_t V_{S1} \end{aligned}$$

Series

when n transistor in series

the equivalent transistor has the same width
but $n \cdot L$

$$\left(\frac{W}{L}\right)_{eq} = \frac{W}{n \cdot L}$$

b) $I_{tot} = I_1 + I_2 + I_3 + \dots + I_N$
 $= A \cdot \frac{w_1}{L_1} + A \cdot \frac{w_2}{L_2} + A \cdot \frac{w_3}{L_3} + \dots + A \cdot \frac{w_N}{L_N}$

since W is different, but same Length

$$I_{tot} = A \cdot \left(\frac{\sum_{n=1}^N w_n}{L} \right) = A \cdot \frac{w_1}{L} + A \cdot \frac{w_2}{L} + \dots + A \left(\frac{w_1 + w_2 + \dots + w_N}{L} \right)$$

Replace all transistors with single one

$$I_{tot} = A \cdot \left(\frac{W}{L} \right)_{eq} = A \cdot \frac{\sum_{n=1}^N w_n}{L}$$

$$so \boxed{\left(\frac{W}{L} \right)_{eq} = \frac{\sum_{n=1}^N w_n}{L}}$$

c) Different L , but same W

$$\left(\frac{w}{L}\right)_{eq} = \frac{W}{\sum_{n=0}^N L_n}$$

25

5. Switches [20 pts]

- We often need to use transistors as switches in circuits. In particular, a whole class of discrete-time circuits relies on making good switches. Your supervisor at Triton Industries has asked you to make and characterize some switches for their upcoming design.
- Derive an expression as a function of W/L for the "on-resistance" of an NMOS switch with the gate tied to V_{DD} . (Note: Neglect the body effect.) Use a $V_{DD} = 1.8V$ and $L = 500\text{ nm}$.
 - Using Cadence, sweep V_S from $-V_{DD}/2$ to $V_{DD}/2$ and W/L with $V_G = V_{DD}$ and $V_B = V_{DD}/2$. The body should be tied to V_{SS} and $L = 500\text{ nm}$. How should you size the switch if you want the on-resistance to be less than $1\text{ k}\Omega$ across the entire range? Submit your schematic and simulation results. (Hint: You need to do two sweeps! Re-read the tutorial if you are unsure how to do this.)
 - Repeat (a) - (b) using a PMOS. Use $V_G = 0\text{ V}$ instead of V_{DD} and $V_B = V_{DD}$. Assume $|V_B| = V_t$.
 - Repeat (a) - (b) using an NMOS and PMOS in parallel. Size the PMOS k times larger where k is the ratio between parts (b) and (c). Explain where this ratio arises from. Use the correct V_G for each transistor.


when use
transistors as switches,
transistor are usually
in triode region

a)

$$R_{ON} = \frac{V_{DS}}{i_D} \quad V_{GS} = V_{DS}$$

$$V_{GS} = V_{DD}$$

$$V_{DS} = V_{DD}$$

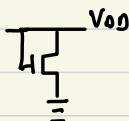


$$I_D = \frac{1}{2} k' n \frac{w}{L} (V_{DD}V_{DS} - \frac{1}{2} V_{DS}^2)$$

Assuming $V_{DS} \ll 1$, so 2nd term can be neglected

$$i_D = k' n \frac{w}{L} V_{DD} \cdot V_{DS} \quad V_{DD} = V_{GS} - V_{t,n} = 1.8 - 0.9 - 0.5$$

$$R_{ON} = \frac{V_{DS}}{i_D} = \frac{1}{k' n \frac{w}{L} \cdot V_{DD}} = \frac{1}{k' n \frac{w}{L} \cdot V_{DD}}$$


b)

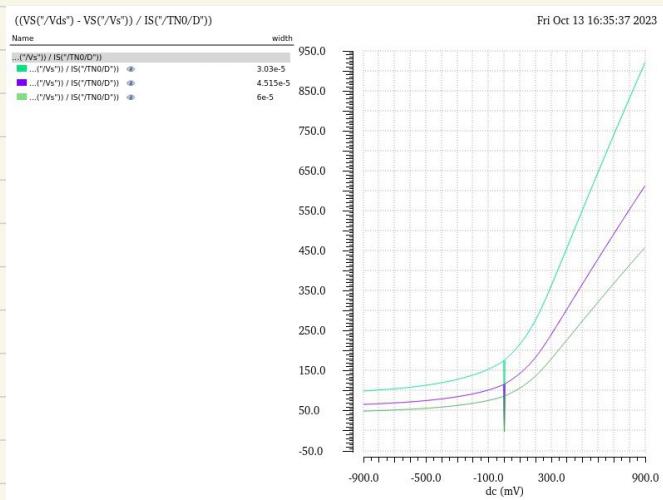


$$W = 3.03 \times 10^{-5}$$

satisfy the requirement

$$= 0.0303 \text{ m}$$

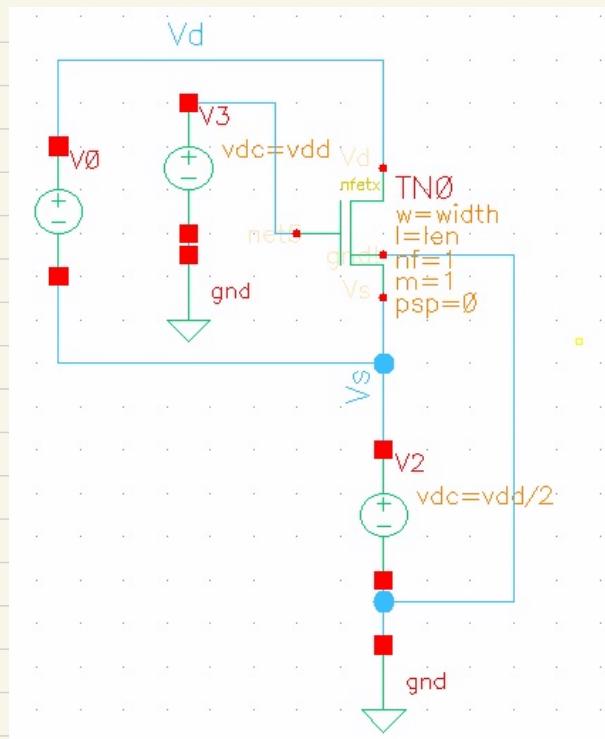


c)

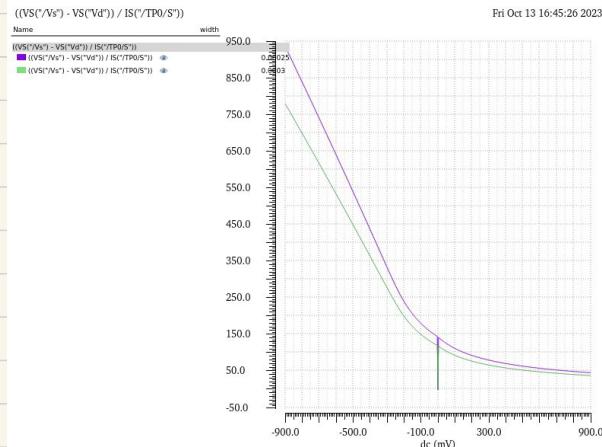

$W = 0.00025$
satisfy the
requirement

$$= 0.25 \text{ m}$$

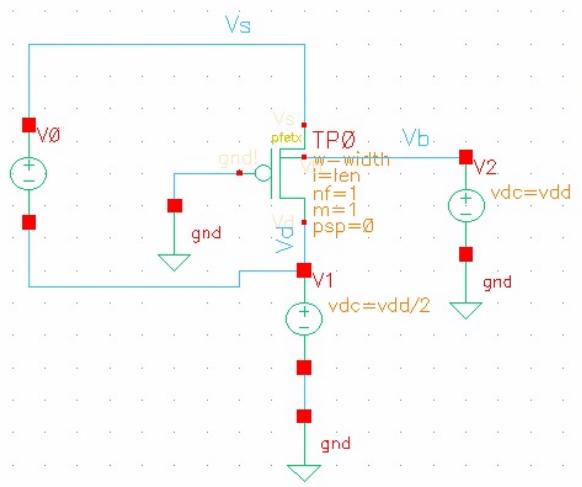

$$i_D = k'_p \frac{W}{L} \left(V_{OV} v_{SD} - \frac{1}{2} v_{SD}^2 \right)$$

$$i_0 = k'_p \frac{w}{L} (V_{ov} v_{so})$$

$$R_{on} = \frac{V_{so}}{i_0} = \boxed{\frac{1}{k'_p \frac{w}{L} \cdot V_{ov}}}$$

Assuming $V_{so} \ll 1$
the 2nd term can be
neglect

$$d) R = \frac{0.25m}{0.0303m} \approx 8.25$$

Assuming $V_{SD} \ll 1$, $V_{GS} \ll 1$
and both are in triode region. 2nd term can be neglected

$i_{D,n}$	$i_{D,p}$
$k'_n \left(\frac{w}{l}\right)_n \cdot V_{GS} u_{DS}$	$k'_p \left(\frac{w}{l}\right)_p \cdot V_{GS} u_{SD}$

$$8.25 \left(\frac{w}{l}\right)_n = \left(\frac{w}{l}\right)_p$$

$$R_{on} = \frac{u_{DS}}{i_D} = \frac{u_{SD}}{i_D}$$

$$R_{on,n} = \frac{1}{k'_n \left(\frac{w}{l}\right)_n \cdot 0.4}$$

$$= \frac{5}{2} \frac{1}{k'_n \left(\frac{w}{l}\right)_n}$$

$$R_{on,p} = \frac{1}{k'_p \left(\frac{w}{l}\right)_p \cdot V_{GS}} = \frac{1}{k'_p \left(\frac{w}{l}\right)_p \cdot 8.25 \cdot 1.3}$$



$$= \frac{40}{429} \frac{1}{k'_p \left(\frac{w}{l}\right)_p}$$

$$R_{eq} = R_{on,n} || R_{on,p}$$

$$= \frac{1}{\frac{5}{2} \frac{1}{k'_n \left(\frac{w}{l}\right)_n} + \frac{40}{429} \frac{1}{k'_p \left(\frac{w}{l}\right)_p}} = \frac{1}{\frac{2}{5} k'_n \left(\frac{w}{l}\right)_n + \frac{429}{40} k'_p \left(\frac{w}{l}\right)_p}$$

where this ratio arises from?

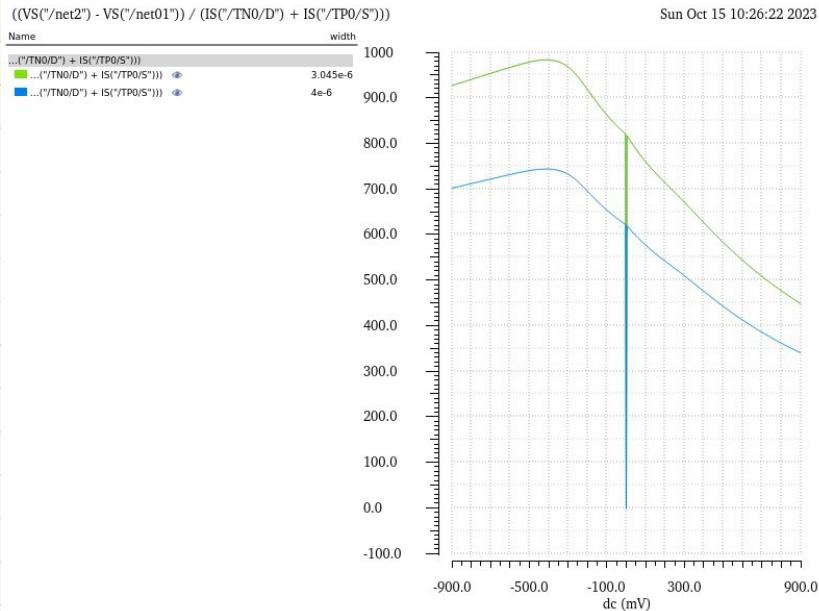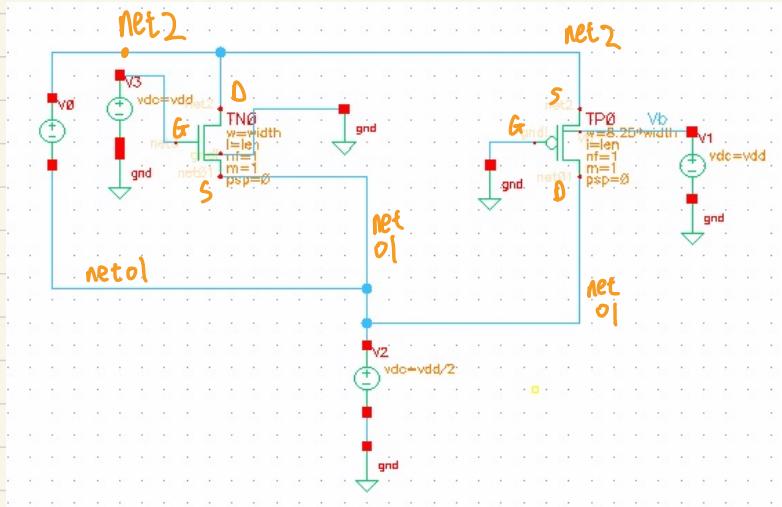In the PMOS, the mobility of holes is less than the mobility of electrons. In order to maintain the same current across transistors, PMOS need to have wider width to maintain the same current as NMOS.



② Width = 3.045 μm while Length = 500 nm
the $R_{on} < 1k$ across the entire range